



---

**(Papers) SSC Junior Engineer Exam Paper - 2016 "held on 04 March 2017 "Afternoon Shift( General Engineering)**

---

**QID : 601** - A current is said to be alternating when it changes in \_\_\_\_\_.

**Options:**

- 1) Magnitude only
- 2) Direction only
- 3) Both magnitude and direction
- 4) None of these

**Correct Answer:** Both magnitude and direction

**QID : 602** - The rms value of a sine wave is 100 A. Its peak value is \_\_\_\_\_.

**Options:**

- 1) 70.7 A
- 2) 141.4 A
- 3) 150 A
- 4) 282.8 A

**Correct Answer:** 141.4 A

**QID : 603** - A 50 Hz ac voltage is measured with a moving iron voltmeter and a rectifier type ac voltmeter connected in parallel. If the meter readings are  $V_1$  and  $V_2$  respectively and the meters are free from calibration errors, then the form factor of the ac voltage may be estimated as \_\_\_\_\_.

**Options:**

- 1)  $V_1/V_2$
- 2)  $1.11 V_1/V_2$
- 3)  $2 V_1/V_2$
- 4)  $\pi V_1/2V_2$

**Correct Answer:**  $1.11 V_1/V_2$

**QID : 604** - The rms value of the resultant current in a wire which carries a dc current of 10 A and a sinusoidal alternating current of peak value 20 A is \_\_\_\_\_.

**Options:**

- 1) 14.1 A
- 2) 17.3 A
- 3) 22.4 A
- 4) 30 A

**Correct Answer:** 17.3 A

**QID : 605** - Two sinusoidal emfs are given as \_\_\_\_\_.  $e_1=A \sin(\omega t+\pi/4)$  and  $e_2=B \sin(\omega t-\pi/6)$ . The phase difference between the two quantities, in degrees, is \_\_\_\_\_.

**Options:**

- 1) 75
- 2) 105
- 3) 60
- 4) 15

**Correct Answer:** 75

**QID : 606** - Which of the following statements pertains to resistor only?

**Options:**


- 1) they oppose sudden changes in voltages
- 2) they can act as energy storage devices
- 3) they can dissipate desirable amount of power
- 4) None of these

**Correct Answer:** they can dissipate desirable amount of power

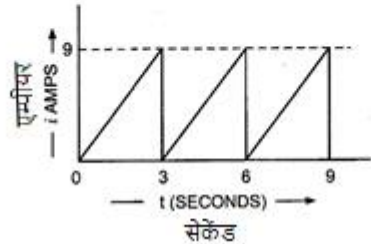**QID : 607 -**

The current waveform in a pure resistor of  $10 \Omega$  is shown in the given figure. Power dissipated in the resistor is:-

$10 \Omega$  के शुद्ध प्रतिरोध का धारा तरंगरूप आकृति में दर्शाया गया है। प्रतिरोध में निष्पादित शक्ति होगी :



**Options:**

- 1) 7.29 W
- 2) 52.4 W
- 3) 135 W
- 4) 270 W

**Correct Answer:** 270 W

**QID : 608 -** Purely inductive circuit takes power from the ac mains when \_\_\_\_\_.

**Options:**

- 1) both applied voltage and current increase
- 2) both applied voltage and current decrease
- 3) applied voltage decreases but current increases
- 4) applied voltage increases but current decreases

**Correct Answer:** applied voltage decreases but current increases

**QID : 609 -** A pure capacitance connected across 50 Hz, 230 V supply consumes 0.04 W. This consumption is attributed to \_\_\_\_\_.

**Options:**

- 1) ohmic loss due to ohmic resistance of plates
- 2) loss of energy in dielectric
- 3) capacitive reactance in ohms
- 4) Both ohmic loss due to ohmic resistance of plates and loss of energy in dielectric

**Correct Answer:** Both ohmic loss due to ohmic resistance of plates and loss of energy in dielectric

**QID : 610** - A voltage of  $50\sin 1000t$  V is applied across a parallel plate capacitor with plate area of  $5\text{ cm}^2$  and plate separation gap of  $5\text{ mm}$ . If the dielectric material in the capacitor has  $\epsilon = 2\epsilon_0$ , then the capacitor current in (Amperes) will be \_\_\_\_\_.

**Options:**


- 1)  $[104/\epsilon_0]\cos 103t$
- 2)  $\epsilon_0 104\cos 103t$
- 3)  $[104/\epsilon_0]\sin 103t$
- 4)  $\epsilon_0 104\sin 103t$

**Correct Answer:**  $\epsilon_0 104\cos 103t$

**QID : 611** -

For the AC circuit as shown below, if the rms voltage across the resistor is  $120\text{ V}$ , what is the value of the inductor?

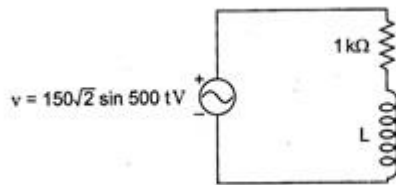नीचे दिये अनुसार एसी परिपथ के लिए, यदि प्रतिरोध के साथ आरएमएस वोल्टेज  $120\text{V}$  हो, तो प्रेरित्र का मान क्या होगा?



**Options:**


- 1)  $0.5\text{ H}$
- 2)  $0.6\text{ H}$
- 3)  $1\text{ H}$
- 4)  $1.5\text{ H}$

**Correct Answer:**  $1.5\text{ H}$

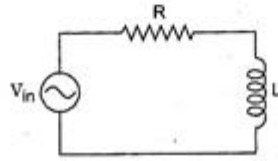**QID : 612 -**

The R-L circuit of the figure is fed from a constant magnitude variable frequency sinusoidal voltage source  $v_{in}$ . At 100 Hz, the R and L element each has a voltage drop  $U_{rms}$ . If the frequency of the source is changed to 50 Hz, then new voltage drop across R is:-

आकृति में R-L परिपथ को अचर परिमाण, चर आवृत्ति ज्यावक्रिय वोल्टेज स्रोत  $v_{in}$  से आपूर्ति की जाती है। 100 हर्ट्ज पर, R और L दोनों में वोल्टेज ड्रॉप  $U_{rms}$  होता है। यदि स्रोत की आवृत्ति 50 हर्ट्ज बदल जाए तो R के साथ वोल्टेज ड्रॉप \_\_\_\_\_ होगा:-



**Options:**

1)

$$\sqrt{\frac{5}{8}} U_{rms}$$

2)

$$\sqrt{\frac{2}{3}} U_{rms}$$

3)

$$\sqrt{\frac{8}{5}} U_{rms}$$

4)

$$\sqrt{\frac{3}{2}} U_{rms}$$

**Correct Answer:**

$$\sqrt{\frac{8}{5}} U_{rms}$$

**QID : 613 -** A certain R-L series combination is connected across a 50 Hz single-phase ac supply. If the instantaneous power drawn was found to be negative for 2 milliseconds in one cycle, the power factor angle of the circuit must be \_\_\_\_\_.

**Options:**

1)  $9^\circ$

# SSC Junior Engineer Exam Printed Study Kit



- 100% Syllabus Covered (Paper-1)
- 3 Books, 500+ Pages
- 2,000+ MCQs
- 5 Practice Tests (PDF Copy)
- 1 Year Current Affairs (PDF Copy)

**50%**  
OFF

~~₹ 3,000/-~~  
**₹ 1,499/-**

FREE  
SHIPPING 

[Click Here for More Details](#)

[SSCPORTAL.IN](http://SSCPORTAL.IN)

## What you will get:

- 100% Syllabus Covered
- 5 Booklets (Paper-1)
- 520+ Pages
- 2,000+ MCQs
- Five Practice Papers
- One Year Current Affairs
- Guidance & Support from Our Experts

Price of the Kit:

~~Rs. 3,000~~

**Rs. 1,499/-**

*(Limited time Offer)*

 [Buy Online](#)

Net Banking

[FOR MORE DETAILS CLICK HERE](#)

[Order Online \(100% Safe\)](#)

[Click here for Other Payment Options \(Cash/NEFT/etc\)](#)

**50%**  
**OFF**

[CLICK HERE](#)

2)  $18^\circ$

3)  $36^\circ$

4)  $45^\circ$

**Correct Answer:**  $36^\circ$

**QID : 614** - The voltage phasor of a circuit is  $10\angle 15^\circ\text{V}$  and the current phasor is  $2\angle -45^\circ\text{A}$ . The active and reactive powers in the circuit are \_\_\_\_\_.

**Options:**

1) 10 W and 17.32 VAR

2) 5 W and 8.66 VAR

3) 20 W and 60 VAR

4)  $20\sqrt{2}$  W and  $10\sqrt{2}$  VAR

**Correct Answer:** 10 W and 17.32 VAR

**QID : 615** - In an RLC circuit, supplied from an ac source, the reactive power is proportional to the

**Options:**

1) average energy stored in the electric field

2) average energy stored in the magnetic field

3) sum of the average energy stored in the electric field and that stored in the magnetic field

4) difference between the average energy stored in the electric field and that stored in the magnetic field

**Correct Answer:** difference between the average energy stored in the electric field and that stored in the magnetic field

**QID : 616** - In gases the flow of current is due to \_\_\_\_\_.

**Options:**

1) Electrons only

2) Positive and negative ions

3) Electrons, positive ions

4) Electrons, positive ions and negative ions

**Correct Answer:** Electrons, positive ions and negative ions

**QID : 617** - Ohm's law is applicable to \_\_\_\_\_.

**Options:**

1) semiconductors

- 2) vacuum tubes
- 3) electrolytes
- 4) None of these

**Correct Answer:** None of these

**QID : 618** - Pure metals generally have \_\_\_\_\_.

**Options:**

- 1) high conductivity and low temperature coefficient
- 2) high conductivity and large temperature coefficient
- 3) low conductivity and zero temperature coefficient
- 4) low conductivity and high temperature coefficient

**Correct Answer:** high conductivity and large temperature coefficient

**QID : 619** - The insulation resistance of a cable of length 10 km is 1 M $\Omega$ . For a length of 100 km of same cable, the insulation resistance will be \_\_\_\_\_.

**Options:**


- 1) 1 M $\Omega$
- 2) 10 M $\Omega$
- 3) 0.1 M $\Omega$
- 4) 0.01 M $\Omega$

**Correct Answer:** 0.1 M $\Omega$

**QID : 620** -

All the resistances in figure shown below are 1  $\Omega$  each. The value of current 'I' is:-

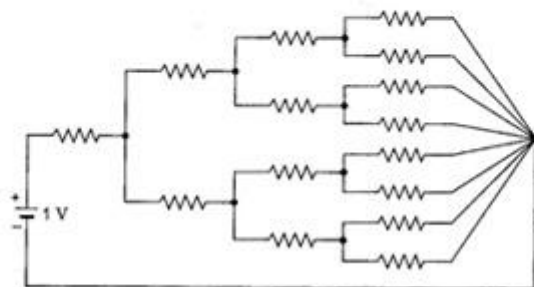दर्शाई गई आकृति में सभी प्रतिरोध 1  $\Omega$  के हैं। धारा 'I' का मान \_\_\_\_\_ होगा:-





**Options:**

1)  $1/15$  A

2)  $2/15$  A

3)  $4/15$  A

4)  $8/15$  A

**Correct Answer:**  $8/15$  A

**QID : 621** - Which of the following does not use heating effect of electric current?

**Options:**

1) Electric furnace

2) Geyser

3) Electric iron


4) Vacuum cleaner

**Correct Answer:** Vacuum cleaner

**QID : 622** -

In the figure given below, the value of:-

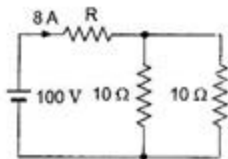नीचे दी आकृति में, R का मान \_\_\_\_ होगा :-



**Options:**

1)  $2.5 \Omega$

2)  $5 \Omega$

3)  $7.5 \Omega$

4)  $10 \Omega$

**Correct Answer:**  $7.5 \Omega$

**QID : 623** - Four 100 W bulbs are connected in parallel across 200 V supply line. If one bulb gets fused \_\_\_\_\_.

**Options:**

- 1) no bulb will light
- 2) all the four bulbs will light
- 3) rest of the three bulbs will light
- 4) None of these

**Correct Answer:** rest of the three bulbs will light

**QID : 624** - A 100 watt light bulb burns on an average of 10 hours a day for one week. The weekly consumption of energy will be \_\_\_\_\_.

**Options:**

- 1) 7 units
- 2) 70 units
- 3) 0.7 units
- 4) 0.07 units

**Correct Answer:** 7 units

**QID : 625** - The elements which are not capable of delivering energy by its own are known as \_\_\_\_\_.

**Options:**

- 1) unilateral elements
- 2) nonlinear elements
- 3) passive elements
- 4) active elements

**Correct Answer:** passive elements

**QID : 626** - A network has 4 nodes and 3 independent loops. What is the number of branches in the network?

**Options:**

- 1) 5
- 2) 6
- 3) 7
- 4) 8

**Correct Answer:** 6

**QID : 627** - A connected network of  $N > 2$  nodes has at most one branch directly connecting any pair of nodes. The graph of the network \_\_\_\_\_.

$N > 2$  \_\_\_\_\_ (\_\_\_\_\_) \_\_\_\_\_  
\_\_\_\_\_ \_\_\_\_\_  
\_\_\_\_\_ \_\_\_\_\_

**Options:**

- 1) must have at least  $N$  branches for one or more closed paths to exist
- 2) can have an unlimited number of branches
- 3) can only have at most  $N$  branches
- 4) can have a minimum number of branches not decided by  $N$

**Correct Answer:** must have at least  $N$  branches for one or more closed paths to exist

**QID : 628** -

The determinant of the matrix  $\begin{bmatrix} 1 & 0 & 0 & 0 \\ 100 & 1 & 0 & 0 \\ 100 & 200 & 1 & 0 \\ 100 & 200 & 300 & 1 \end{bmatrix}$  is:-

आव्यूह  $\begin{bmatrix} 1 & 0 & 0 & 0 \\ 100 & 1 & 0 & 0 \\ 100 & 200 & 1 & 0 \\ 100 & 200 & 300 & 1 \end{bmatrix}$  का सारणिक \_\_\_\_\_ होगा:-

**Options:**

- 1) 100
- 2) 200
- 3) 1
- 4) 300

**Correct Answer:** 1

**QID : 629** - Ideal voltage source have \_\_\_\_\_.

**Options:**

- 1) zero internal resistance

- 2) infinite internal resistance
- 3) low value of current
- 4) large value of emf

**Correct Answer:** zero internal resistance

**QID : 630** - A voltage source having an open circuit voltage of 100 V and internal resistance of 50  $\Omega$  is equivalent to a current source \_\_\_\_\_.

**Options:**


- 1) 2 A in parallel with 50  $\Omega$
- 2) 2 A in series with 50  $\Omega$
- 3) 0.5 A in parallel with 50  $\Omega$
- 4) 2 A in parallel with 100  $\Omega$

**Correct Answer:** 2 A in parallel with 50  $\Omega$

**QID : 631** -

Consider the circuit given below. What is the power delivered by the 24 V source?

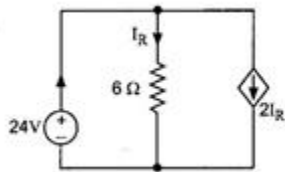नीचे दिये परिपथ पर विचार कीजिये । 24V स्रोत द्वारा दी जाने वाली शक्ति कितनी होगी?



**Options:**

- 1) 96 W
- 2) 114 W
- 3) 192 W
- 4) 288 W

**Correct Answer:** 288 W

# SSC Constable (GD) Exam Study Kit



- ▶ 100% Written Exam Syllabus
- ▶ 700+ Pages, Printed Books
- ▶ 1500 MCQ, 8 Books
- ▶ Practice Question Papers
- ▶ 1 Year Current Affairs

**50% OFF**  
~~₹ 3,200/-~~  
**₹ 1599/-**



for Exam Help Call Us at: +91 8800734161

IAS EXAM PORTAL

## What you will get:

- 100% Syllabus Covered
- 8 Booklets
- 700+ Pages
- Five Practice Papers
- One Year Current Affairs
- Current Affairs for Exam
- Guidance & Support from Our Experts

Price of the Kit:

~~Rs. 3,200~~

**Rs. 1,599/-**  
(Limited time Offer)



Net Banking

**Order Online (100% Safe)**

[Click here for Other Payment Options \(Cash/NEFT/etc\)](#)


[FOR MORE DETAILS CLICK HERE](#)



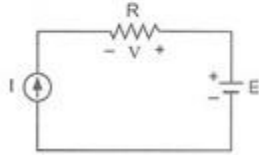**QID : 632 -**

For the circuit shown what is the voltage  $V$  if the source voltage is reduced by 50%?

नीचे दिये परिपथ के लिए स्रोत वोल्टेज को 50% कम करने पर वोल्टेज  $V$  कितनी होगी?



**Options:**

- 1)  $IR + E$
- 2)  $E - IR$
- 3)  $2IR - (E/2)$
- 4)  $(E/2) - IR$

**Correct Answer:**  $(E/2) - IR$

**QID : 633 -** A coil wound over an iron carries certain current and establishes flux in the ring. If the area of a x-section of the ring is doubled, the flux density in the core \_\_\_\_\_.

**Options:**

- 1) is double of the previous value
- 2) is half of the previous value
- 3) is same as the previous value
- 4) is not possible to predict

**Correct Answer:** is half of the previous value

**QID : 634 -** A cast steel electromagnet has an air gap length of 0.3 cm. Find the ampere-turns for the air gap to produce a flux density of 0.7 Wb/m<sup>2</sup> in the air gap.

**Options:**

- 1) 2100 AT
- 2) 1671 AT
- 3) 1447 AT
- 4) 167 AT

**Correct Answer:** 1671 AT

**QID : 635** - An air gap is usually inserted in magnetic circuits so as to \_\_\_\_\_.

**Options:**

- 1) prevent saturation
- 2) increase mmf
- 3) increase in flux
- 4) increase in inductance

**Correct Answer:** prevent saturation

**QID : 636** - Which of the following statements is correct?

**Options:**

- 1) The magnetic flux inside the exciting coil is the same as on its outer surface
- 2) The magnetic flux inside an exciting coil is zero
- 3) The magnetic flux inside the exciting coil is greater than that on its outside surface
- 4) The magnetic flux inside the exciting coil is lower than that on the outside surface

**Correct Answer:** The magnetic flux inside the exciting coil is the same as on its outer surface

**QID : 637** - Consider the following statements:

The force per unit length between two stationary parallel wires carrying (steady) currents \_\_\_\_\_.

- A. is inversely proportional to the separation of wires.
- B. is proportional to the magnitude of each current.
- C. satisfies Newton's third law.

Out of these \_\_\_\_\_.

**Options:**

- 1) A and B are correct
- 2) B and C are correct
- 3) A and C are correct
- 4) A, B and C are correct

**Correct Answer:** A, B and C are correct

---

**QID : 638** - A magnetic circuit requires 800 AT to produce a certain quantity of flux in magnetic circuit. If its excitation coil has 100 turns and 5 ohm resistance, the voltage to be applied in exciting coil is \_\_\_\_\_.

**Options:**

1) 60 V

2) 40 V

3) 80 V

4) 8 V

**Correct Answer:** 40 V

**QID : 639** - According to Faraday's law of electromagnetic induction an emf is induced in a conductor whenever it \_\_\_\_\_.

**Options:**

1) lies in a magnetic field

2) lies perpendicular to the magnetic field

3) cuts the magnetic flux

4) moves parallel to the direction of magnetic field

**Correct Answer:** cuts the magnetic flux

**QID : 640** - "In all cases electromagnetic induction, an induced voltage will cause a current to flow in a closed circuit in such a direction that the magnetic field which is caused by that current will oppose the change that produces the current", is the original statement of \_\_\_\_\_.

**Options:**

1) Lenz's law

2) Faraday's law of magnetic induction

3) Fleming's law of induction

4) Ampere's law

**Correct Answer:** Lenz's law

**QID : 641** - A 500 kVA transformer has constant loss of 500 W and copper losses at full load are 2000 W. Then at what load, is the efficiency maximum?

**Options:**

1) 250 KVA

2) 500 kVA

3) 1000 kVA



4) 125 kVA

**Correct Answer:** 250 KVA

**QID : 642** - The all day efficiency of a transformer depends primarily on \_\_\_\_\_.

**Options:**

- 1) its copper losses
- 2) the amount of load
- 3) the duration of load
- 4) Both the amount and duration of load

**Correct Answer:** Both the amount and duration of load

**QID : 643** - In a power transformer, the breather is provided in order to \_\_\_\_\_.

**Options:**

- 1) filter transformer oil
- 2) prevent ingress of moisture with air
- 3) the cooling oil
- 4) provide fresh air for increasing cooling effect

**Correct Answer:** prevent ingress of moisture with air

**QID : 644** - The stator core of a synchronous machine is built up of \_\_\_\_\_ laminations.

**Options:**

- 1) stainless steel
- 2) silicon steel
- 3) cast iron
- 4) cast steel

**Correct Answer:** silicon steel

**QID : 645** - The sag of a transmission line conductor in summer is \_\_\_\_\_.

**Options:**

- 1) less than that in winter
- 2) more than that in winter
- 3) same as in winter
- 4) None of these

**Correct Answer:** more than that in winter

**QID : 646** - The slip rings employed in a 3-phase synchronous machine are insulated for \_\_\_\_\_.

**Options:**

- 1) output rated voltage
- 2) low voltage

- 3) very low voltage
- 4) very high voltage

**Correct Answer:** low voltage

**QID : 647** - For a linear electromagnetic circuit, which of the following statement is true?

**Options:**

- 1) Field energy is equal to the co-energy
- 2) Field energy is greater than the co-energy
- 3) Field energy is lesser than the co-energy
- 4) Co-energy is zero

**Correct Answer:** Field energy is equal to the co-energy

**QID : 648** - A short circuited rectangular coil falls under gravity with the coil remaining in a vertical plane and cutting perpendicular horizontal magnetic lines of force. It has \_\_\_\_\_ acceleration.

**Options:**

- 1) zero
- 2) increasing
- 3) decreasing
- 4) constant

**Correct Answer:** constant

**QID : 649** - Reluctance torque in rotating machines is present, when \_\_\_\_\_.

**Options:**

- 1) air gap is not uniform
- 2) reluctance seen by stator mmf varies
- 3) reluctance seen by rotor mmf varies
- 4) reluctance seen by the working mmf varies

**Correct Answer:** reluctance seen by the working mmf varies

**QID : 650** - In a dc motor the windage loss is proportional to \_\_\_\_\_.

**Options:**

- 1) supply voltage
- 2) square of the supply voltage
- 3) square of the flux density
- 4) square of the armature speed

**Correct Answer:** square of the armature speed

**QID : 651** - Generally the no-load losses of an electrical machine is represented in its equivalent circuit by a \_\_\_\_\_.

**Options:**

- 1) parallel resistance with a low value
- 2) series resistance with a low value
- 3) parallel resistance with a high value
- 4) series resistance with a high value

**Correct Answer:** parallel resistance with a low value

**QID : 652** - The zero-suppression in recorders implies \_\_\_\_\_.

**Options:**

- 1) recording signals with reference to a point other than the zero
- 2) removing the static component so that rest of the signal is displayed with more expansion
- 3) providing inertia-less components to improve transient response
- 4) designing the recorder for zero error

**Correct Answer:** removing the static component so that rest of the signal is displayed with more expansion

**QID : 653** - Null type recorders are \_\_\_\_\_ recorders.

**Options:**

- 1) potentiometric
- 2) bridge
- 3) LVDT
- 4) Any of these

**Correct Answer:** Any of these

**QID : 654** - In a magnetic tape blanks are provided at the \_\_\_\_\_.

**Options:**

- 1) start of the tape
- 2) middle of the tape
- 3) end of the tape
- 4) start and end of the tape

**Correct Answer:** start and end of the tape

**QID : 655** - If the number of bellows elements is made double and the thickness of the bellows element is made half, the displacement of the element for the same applied pressure would be the \_\_\_\_\_.

**Options:**

- 1) 16 times
- 2) 4 times
- 3) same
- 4) one-fourth

**Correct Answer:** 16 times

**QID : 656** - The meter measuring total flow in a liquid makes use of \_\_\_\_\_.

**Options:**

- 1) planimeter
- 2) variable area meter
- 3) square root extractor
- 4) none of these

**Correct Answer:** planimeter

**QID : 657** - Self-generating type transducers are \_\_\_\_\_ transducers.

**Options:**

- 1) active
- 2) passive
- 3) secondary
- 4) inverse

**Correct Answer:** active

**QID : 658** - A transducer that converts measurand into the form of pulse is called the \_\_\_\_\_ transducers.

**Options:**

- 1) active
- 2) analog
- 3) digital
- 4) pulse

**Correct Answer:** digital

**QID : 659** - High value pot resistance leads to \_\_\_\_\_.

# SSC CHSL (10+2) Printed Study Kit



- 100% CHSL Exam Syllabus Covered
- 5 Books, 1000+ Pages
- 4500+ MCQs
- Solved Papers & Mock Tests (PDF Copy)
- 1 Year Current Affairs (PDF Copy)

**50% OFF**  
₹ 4,000/-  
₹ **1,999/-**

FREE SHIPPING 

for Exam Help Call Us at: +91 8800734161

SSCPORTAL.IN

## What you will get:

- 100% CHSL Exam Syllabus Covered
- 5 Booklets
- More Than 1000+ Pages
- 4500+ MCQs
- Previous Solved Papers
- Current Affairs for Exam
- Guidance & Support from Our Experts

Price of the Kit:

Rs. 4,000

**Rs. 1,999/-**

(Limited time Offer)



Net Banking

**Order Online (100% Safe)**

[Click here for Other Payment Options \(Cash/NEFT/etc\)](#)

[FOR MORE DETAILS CLICK HERE](#)



**Options:**

- 1) low sensitivity
- 2) high sensitivity
- 3) low non-linearity
- 4) less error

**Correct Answer:** high sensitivity

**QID : 660** - In wire wound strain gauges, the change in resistance under strained condition is mainly on account of \_\_\_\_\_.

**Options:**

- 1) change in diameter of wire
- 2) change in the length of wire
- 3) change in both length and diameter of wire
- 4) change in resistivity

**Correct Answer:** change in both length and diameter of wire

**QID : 661** - Which of the following is not an advantage of semiconductor gauges as compared to conventional strain gauges?

**Options:**

- 1) Excellent hysteresis characteristics
- 2) Least sensitive to temperature changes
- 3) High fatigue life
- 4) Smaller size

**Correct Answer:** Least sensitive to temperature changes

**QID : 662** - In a vapour compression system, which of the following units is adversely affected by the presence of moisture?

**Options:**

- 1) evaporator
- 2) expansion valve
- 3) compressor
- 4) condenser

**Correct Answer:** expansion valve

**QID : 663** - The range of horse power of diesel locomotive is \_\_\_\_\_.

**Options:**

- 1) 100 – 500
- 2) 1500 – 2500
- 3) 3000 – 4500
- 4) 4500 – 5000

**Correct Answer:** 1500 – 2500

**QID : 664** - Electric traction in comparison to other traction systems has the advantages of \_\_\_\_\_.

**Options:**

- 1) higher acceleration and braking retardation
- 2) cleanest system and so ideally suitable for the underground and tube railways
- 3) better speed control
- 4) All of these

**Correct Answer:** All of these

**QID : 665** - The method suitable for heating of conducting medium is \_\_\_\_\_.

**Options:**

- 1) Induction heating
- 2) Indirect arc heating
- 3) eddy current heating
- 4) radiant heating

**Correct Answer:** Induction heating

**QID : 666** - The danger of electric shock is maximum \_\_\_\_\_.

**Options:**

- 1) before welding
- 2) during welding
- 3) while inserting electrode into the holder
- 4) after welding

**Correct Answer:** while inserting electrode into the holder

**QID : 667** - Halogen lamps have the advantages of \_\_\_\_\_.

**Options:**

- 1) reduced dimensions of the lamp
- 2) better colour rendition and longer life (about 2000 hours)
- 3) high operating temperature with increased luminous efficiency
- 4) All of these

**Correct Answer:** All of these

**QID : 668** - The primary reason for low power factor is owing to installation of \_\_\_\_\_.

**Options:**

- 1) synchronous motor
- 2) dc motors
- 3) induction motor
- 4) None of these

**Correct Answer:** induction motor

**QID : 669** - The load factor for domestic loads may be taken as \_\_\_\_\_.

**Options:**

- 1) about 85%
- 2) 50 – 60%
- 3) 25 – 50%
- 4) 10 – 15%

**Correct Answer:** 10 – 15%

**QID : 670** - An industrial consumer has a load pattern of 2000 kW 0.8 lag for 12 hours and 1000 kW unity power factor for 12 hours. The load factor is \_\_\_\_\_.

**Options:**

- 1) 0.5
- 2) 0.75
- 3) 0.6
- 4) 2

**Correct Answer:** 0.6

**QID : 671** - Diversity factor is the ratio of \_\_\_\_\_.

**Options:**



- 1) sum of maximum demands of consumers/system maximum demand
- 2) maximum demand of consumers/average demand
- 3) demand of all consumers/average demand
- 4) none of these

**Correct Answer:** sum of maximum demands of consumers/system maximum demand

**QID : 672** - Diversity factor x maximum demand is \_\_\_\_\_.

**Options:**

- 1) average demand
- 2) sum of consumer's maximum demands
- 3) installed capacity
- 4) generated capacity

**Correct Answer:** sum of consumer's maximum demands

**QID : 673** - As per recommendation of ISI the maximum number of points of lights, fans, and socket that can be connected in one sub-circuit is \_\_\_\_\_.

**Options:**

- 1) 8
- 2) 10
- 3) 15
- 4) 20

**Correct Answer:** 10

**QID : 674** - Which of the following wiring is preferred for workshop lighting?

**Options:**

- 1) casing-capping wiring
- 2) Batten wiring
- 3) Concealed conduit wiring
- 4) Surface conduit wiring

**Correct Answer:** Concealed conduit wiring

**QID : 675** - According to fuse law, the current carrying capacity varies as \_\_\_\_\_.

**Options:**

- 1) diameter
- 2) (diameter)1.5
- 3) (diameter)1/2
- 4) 1/(diameter)

**Correct Answer:** (diameter)1.5

**QID : 676** - The loop earth wire used shall not be of size less than \_\_\_\_\_.

**Options:**

- 1) 8 SWG
- 2) 10 SWG
- 3) 20 SWG
- 4) 14 SWG (2.9 mm<sup>2</sup>) or half of the size of the sub-circuit wireQ

**Correct Answer:** 14 SWG (2.9 mm<sup>2</sup>) or half of the size of the sub-circuit wireQ

**QID : 677** - Third pin in a 3-pin plug is provided so as to \_\_\_\_\_.

**Options:**

- 1) provide an earth connection
- 2) provide a 3-phase supply, when required
- 3) provide a spare phase when required
- 4) prevent the plug being reversed in the socket

**Correct Answer:** provide an earth connection

**QID : 678** - Which one of the following is used as an active device in electronic circuits?

**Options:**

- 1) Transformer
- 2) Electric heater
- 3) SCR
- 4) Loudspeaker

**Correct Answer:** SCR

**QID : 679** - A device having characteristics very close to that of an ideal voltage source is \_\_\_\_\_.

**Options:**

- 1) Vacuum diode
- 2) Zener diode

3) Transistor

4) FET

**Correct Answer:** Zener diode

**QID : 680** - For thermionic emission \_\_\_\_\_.

**Options:**

- 1) a material with high work function is preferable
- 2) a material with low work function is preferable
- 3) the work function of the material has no importance
- 4) None of these

**Correct Answer:** a material with low work function is preferable

**QID : 681** - A photocell is illuminated by a small bright source placed 1 m away. When the same source of light is placed two metres away, the electrons emitted by the photocathode \_\_\_\_\_.

**Options:**

- 1) each carry one quarter of their previous energy
- 2) each carry one quarter of their previous moments
- 3) are half as numerous
- 4) are one-quarter as numerous

**Correct Answer:** are one-quarter as numerous

**QID : 682** - In a vacuum tetrode secondary emission is because of emission of \_\_\_\_\_.

**Options:**

- 1) electrons from the filament due to heat energy
- 2) high velocity electrons from the cathode
- 3) electrons from the plate due to bombardment of the fast moving electrons emitted from the cathode
- 4) electrons belonging to the second orbit of the atoms of cathode

**Correct Answer:** electrons from the plate due to bombardment of the fast moving electrons emitted from the cathode

**QID : 683** - Which of the following circuit is mostly used as an amplifier?

**Options:**

- 1) common base circuit because it has high voltage gain
- 2) common emitter circuit because it has high voltage and current gain

- 3) common collector circuit because it has high gain
- 4) common emitter circuit is of a little use because it has extremely low input resistance

**Correct Answer:** common emitter circuit because it has high voltage and current gain

**QID : 684** - In a dc compound motor, 4-point starter provided as \_\_\_\_\_.

**Options:**

- 1) to reduce the field current
- 2) to increase the field current
- 3) not to affect the current flowing through 'Hold on' coil even when the field current changes
- 4) none of these

**Correct Answer:** not to affect the current flowing through 'Hold on' coil even when the field current changes

**QID : 685** - The simplest form of a motor controller is \_\_\_\_\_.

**Options:**

- 1) relay
- 2) toggle switch
- 3) drum switch
- 4) magnetic switch

**Correct Answer:** toggle switch

**QID : 686** - The plugging provides \_\_\_\_\_ braking torque in comparison to rheostatic and regenerative braking systems.

**Options:**

- 1) negligible
- 2) small
- 3) highest
- 4) None of these

**Correct Answer:** highest

**QID : 687** - Dynamic braking is very effective if the dc motor \_\_\_\_\_.

**Options:**

- 1) is series excited
- 2) is shunt excited
- 3) is separately excited
- 4) has cumulative compound excitation

**Correct Answer:** is separately excited

**QID : 688** - In case of dc shunt motors, the regenerative braking is employed when the load \_\_\_\_\_.

**Options:**

- 1) has an overhauling characteristic
- 2) is variable
- 3) is constant
- 4) also acts as braking force

**Correct Answer:** has an overhauling characteristic

**QID : 689** - The variable loss in a dc shunt machine is \_\_\_\_\_.

**Options:**

- 1) iron loss
- 2) shunt field loss
- 3) armature copper loss
- 4) friction and windage loss

**Correct Answer:** armature copper loss

**QID : 690** - In a synchronous generator, a divided winding rotor is preferable to a conventional winding rotor because of \_\_\_\_\_.

**Options:**

- 1) higher efficiency
- 2) increased steady-state stability limit
- 3) higher short circuit ration
- 4) better damping

**Correct Answer:** increased steady-state stability limit

**QID : 691** - The stator winding of an alternator is normally connected in star to eliminate the \_\_\_\_\_ harmonic component of the voltage waveform.

**Options:**

- 1) third
- 2) fifth
- 3) seventh
- 4) None of these

**Correct Answer:** third

**QID : 692** - How can the reactive power delivered by a synchronous generator be controlled?

**Options:**

- 1) by changing the prime mover input
- 2) by changing the excitation
- 3) by changing the direction of rotation
- 4) by changing the prime mover speed

**Correct Answer:** by changing the excitation

**QID : 693** - The armature reaction effect in a synchronous machine depends on \_\_\_\_\_.

**Options:**

- 1) load current
- 2) power factor of the load
- 3) speed of the machine
- 4) both load current and power factor of the load

**Correct Answer:** both load current and power factor of the load

**QID : 694** - A synchronous generator is feeding a zero power factor (lagging) load at rated current. The armature reaction is \_\_\_\_\_.

**Options:**

- 1) magnetizing
- 2) demagnetizing
- 3) cross-magnetizing
- 4) ineffective

**Correct Answer:** demagnetizing

**QID : 695** - A synchronous motor may fail to pull into synchronism owing to \_\_\_\_\_.

**Options:**

- 1) excessive load
- 2) low excitation
- 3) high friction
- 4) Any of the options

**Correct Answer:** Any of the options

**QID : 696** - The rated voltage of a 3-phase power system is given as \_\_\_\_\_.

**Options:**

- 1) rms phase voltage
- 2) peak phase voltage
- 3) rms line to line voltage
- 4) peak line to line voltage

**Correct Answer:** rms line to line voltage

**QID : 697** - Feeder is designed mainly from the point of view of \_\_\_\_\_.

**Options:**

- 1) its current carrying capacity
- 2) voltage drop in it
- 3) operating voltage
- 4) operating frequency

**Correct Answer:** its current carrying capacity

**QID : 698** - 66 kV is suitable for transmission of power over \_\_\_\_\_.

**Options:**

- 1) 30 km
- 2) 60 km
- 3) 120 km
- 4) 200 km

**Correct Answer:** 60 km

**QID : 699** - Which of the following properties has got higher value for aluminium in comparison to that of copper?

**Options:**

- 1) Electrical resistivity
- 2) Melting point
- 3) Thermal conductivity
- 4) Specific gravity

**Correct Answer:** Electrical resistivity

**QID : 700** - ACSR conductors have \_\_\_\_\_.

**Options:**

- 1) all conductors made of aluminium
- 2) outer conductors made of aluminum

3) inner conductors made of aluminum

4) no conductors made of aluminum

**Correct Answer:** outer conductors made of aluminum





# SSC EXAMS PRINTED STUDY NOTES

<a href="#">Study Material for SSC CGL (Tier-1) Examination</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for SSC CGL (Tier-2) Exam</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for SSC CHSL (10+2) Examination</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for SSC Stenographers (Grade 'C' &amp; 'D')</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for Multitasking (Non-Technical) - MTS</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for SSC Constables (GD) Exam</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit For SSC Sub-Inspectors in Delhi Police, CAPFs, CISF</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for SSC Junior Engineer Exam (Paper-1)</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<b>IAS EXAMS STUDY MATERIALS</b>		
<a href="#">Study Kit for IAS (Pre) GENERAL STUDIES Paper-1 (GS)</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">Study Kit for IAS (Pre) CSAT Paper-2(Aptitude)</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">सामान्य अध्ययन (GS) प्रारंभिक परीक्षा (Pre) पेपर-1</a>	<a href="#">हिन्दी</a>	<a href="#">CLICK HERE</a>
<a href="#">आई. ए. एस. (सी-सैट) प्रारंभिक परीक्षा पेपर -2</a>	<a href="#">हिन्दी</a>	<a href="#">CLICK HERE</a>
<a href="#">Gist of NCERT Study Kit For UPSC Exams</a>	<a href="#">English</a>	<a href="#">CLICK HERE</a>
<a href="#">यूपीएससी परीक्षा के लिए एनसीईआरटी अध्ययन सामग्री</a>	<a href="#">हिन्दी</a>	<a href="#">CLICK HERE</a>